

Parity Generator & checker

Parity Generator



Let's take 3-bit data

Logic

Even parity bit \rightarrow no. of 1's in data bit even

EP_b

$(EP)_b = 0$ (Remain it even)

\rightarrow no. of 1's in data bit odd

$(EP)_b = 1$ (Make it even)

odd parity bit \rightarrow

OP_b

no. of 1's in data bit even

$(OP)_b = 1$ (Make it odd)

\rightarrow no. of 1's in data bit odd

$(OP)_b = 0$ (Remain it odd)

A	B	C	Even parity
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

A	B	C	odd parity
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Even parity

A \ BC	00	01	11	10
0	0	1	1	1
1	1	1	1	1

$$\Rightarrow \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$\Rightarrow \bar{A}(B \oplus C) + A(B \oplus C)$$

$$\text{Even parity} \Rightarrow A \oplus B \oplus C$$

$$\text{odd parity} = (\text{Even parity})$$

$$\text{odd parity} = \overline{(A \oplus B \oplus C)}$$

Parity checker

Error checker

$$\frac{\text{Even parity Error}}{\text{parity Error}} = 1 \begin{pmatrix} \text{Data} \\ \text{Parity bit} \\ \text{odd 1's} \end{pmatrix}$$

Vice-Versa

$$\frac{\text{Odd parity Error}}{\text{parity Error}} = 1 \begin{pmatrix} \text{Data + parity bit} \\ \text{even 1's} \end{pmatrix}$$

Vice versa even 1's

Data bit

A	B	C	Parity-in	Even parity Error	odd parity Error
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	1

Even parity Error = $(A \oplus B \oplus C \oplus P-in)$

odd parity Error = $\sim (A \oplus B \oplus C \oplus P-in)$